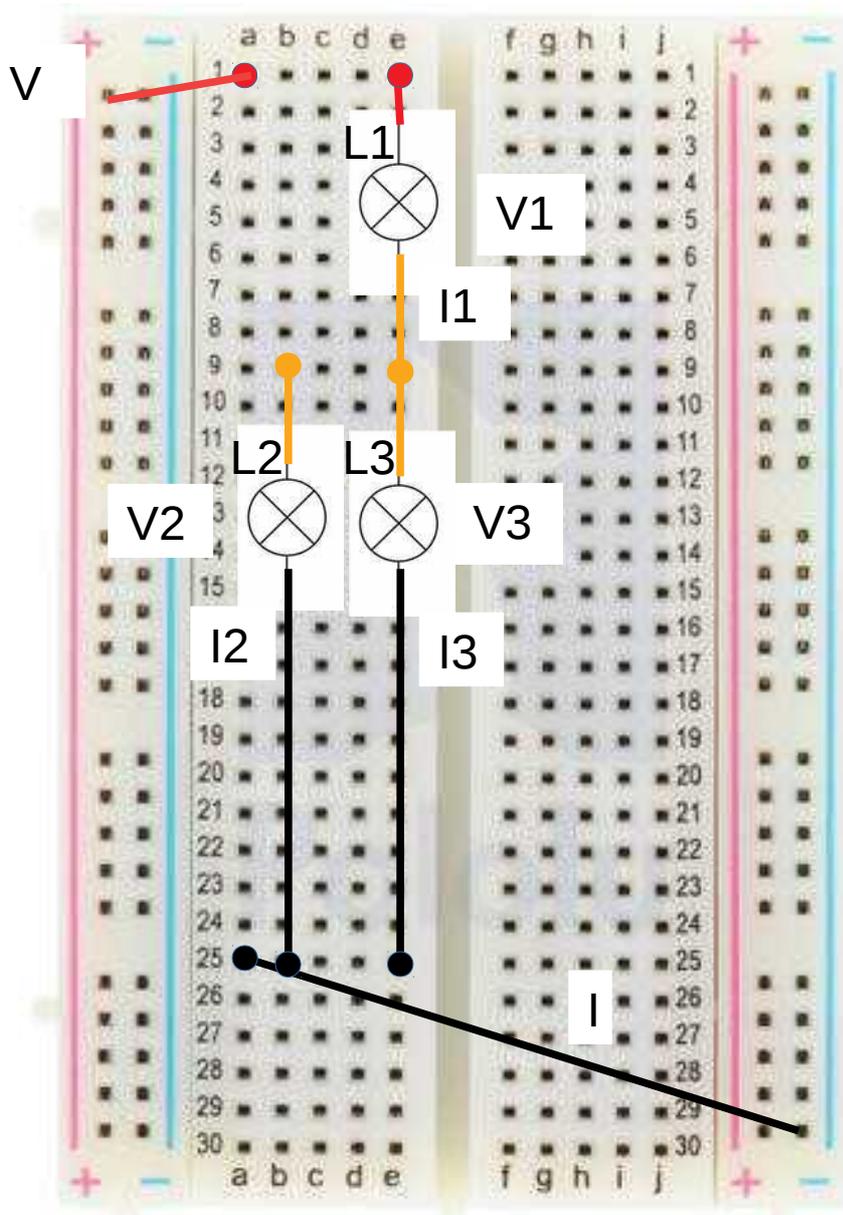


Circuit 1

Nom:




Circuit 1

Circuit 1 - Tensions

Circuit 1 - Intensitats

Circuit 2


Nom:

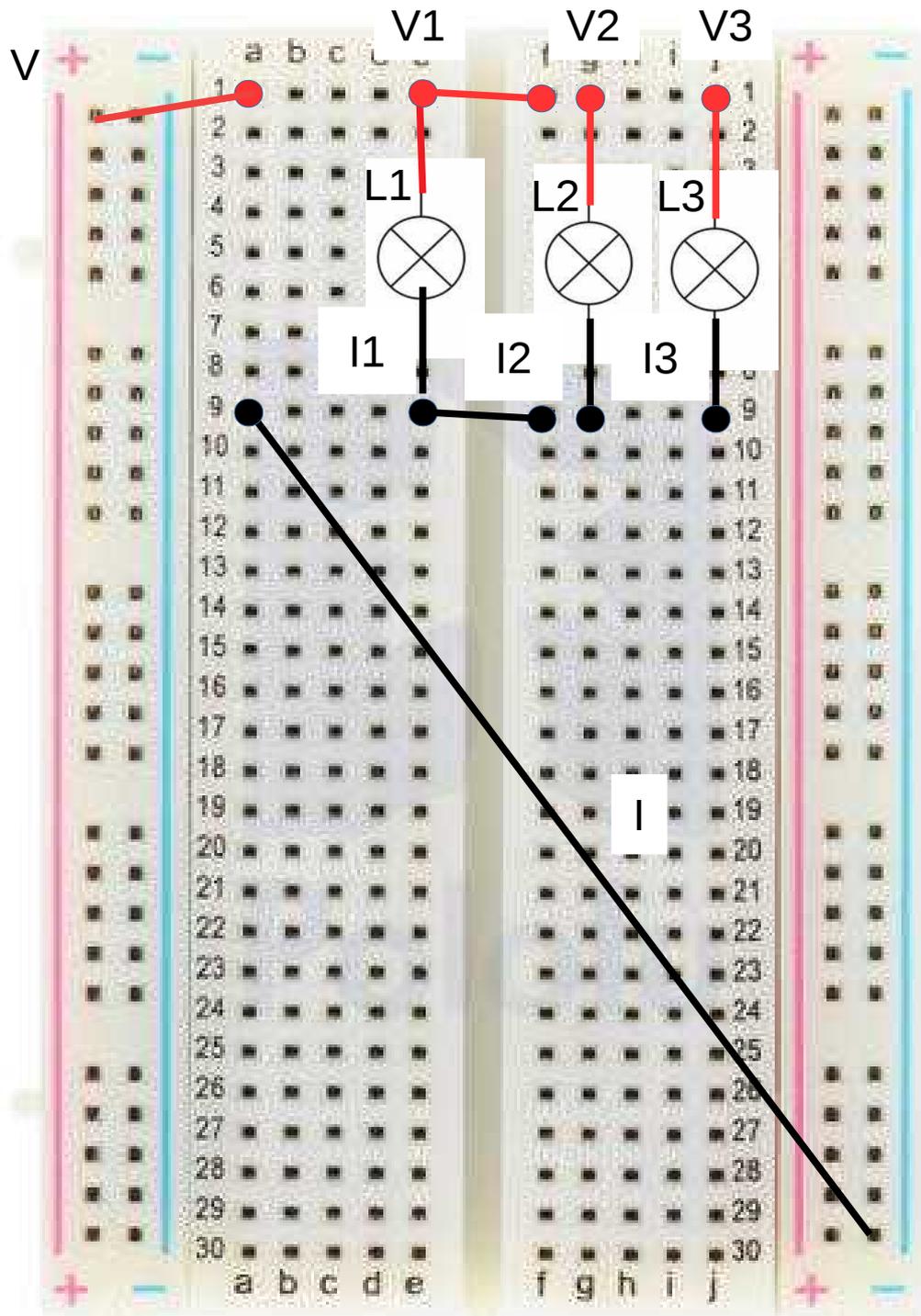

Circuit 2

Circuit 2 - Tensions


Circuit 2 - Intensitats

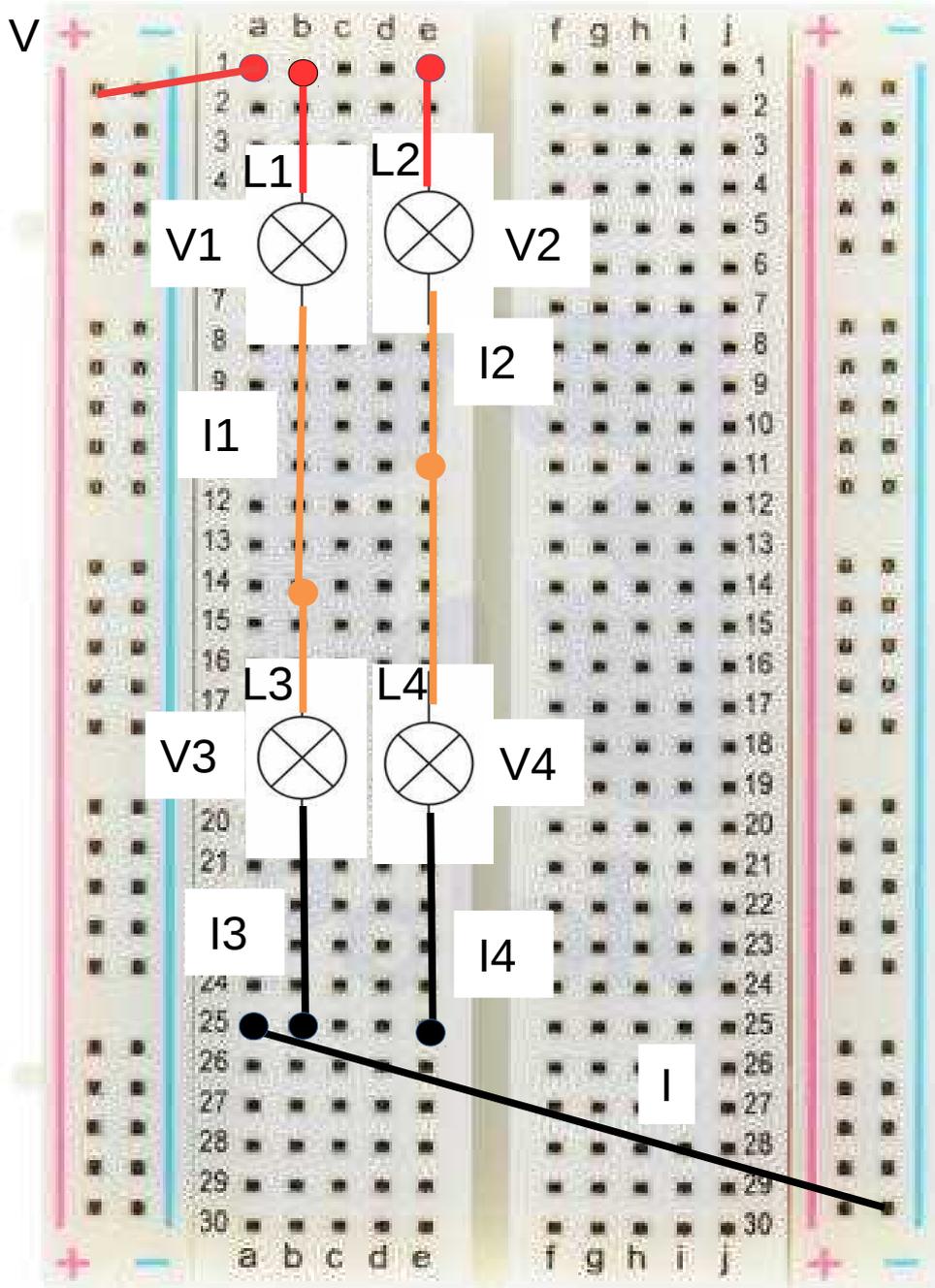

Circuit 3

Circuit 3 - Tensions

Circuit 3 - Intensitats

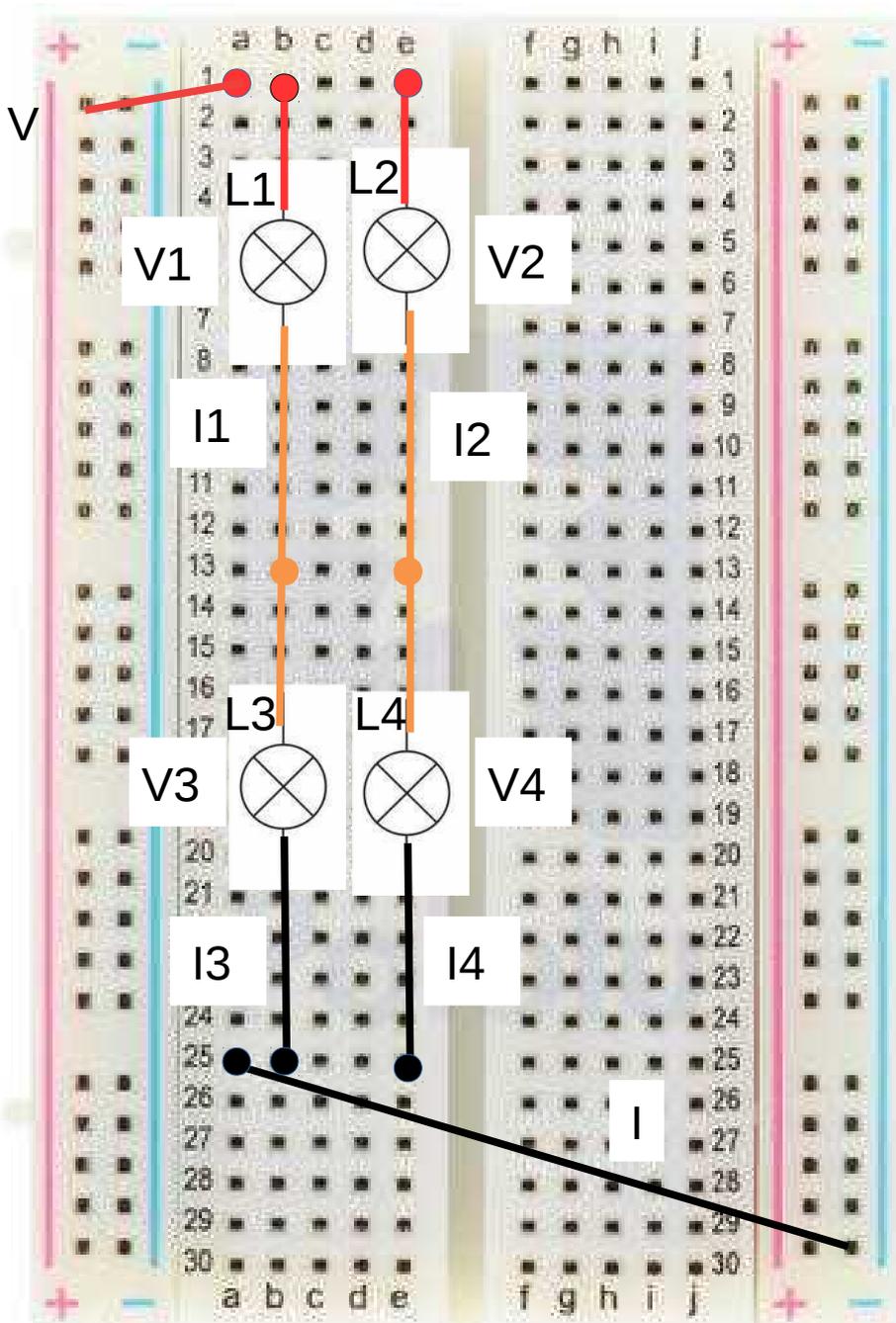


Circuit 4

Circuit 4 - Tensions

Circuit 4 - Intensitats

Circuit 5

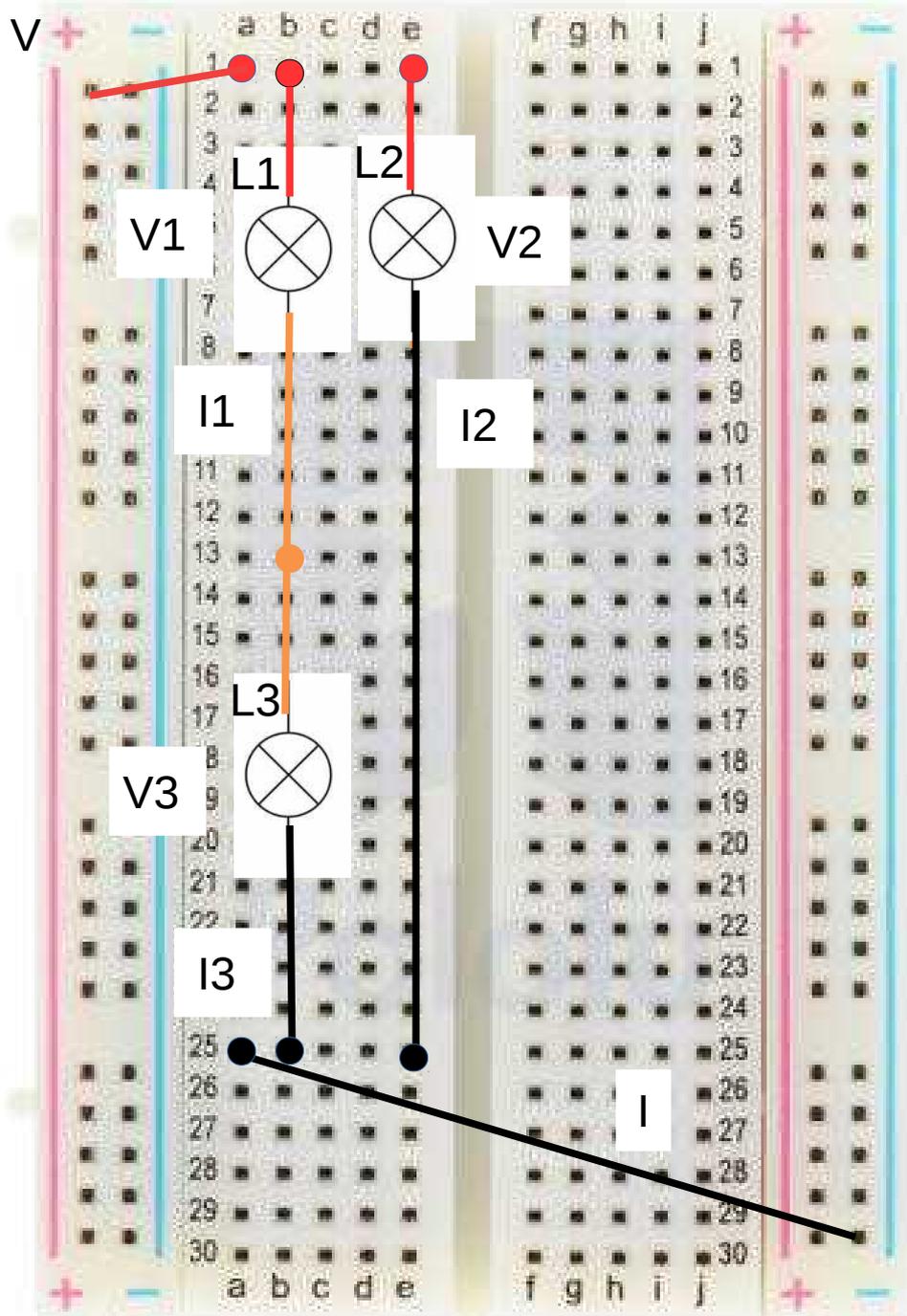

Circuit 5

Circuit 5 - Tensions

Circuit 5 - Intensitats

Circuit n° 1		Nom		
V=	V ₁ =	V ₂ =	V ₃ =	V ₄ =
I=	I ₁ =	I ₂ =	I ₃ =	I ₄ =
R _{eq} =	R ₁ =	R ₂ =	R ₃ =	R ₄ =
P _{eq} =	P ₁ =	P ₂ =	P ₃ =	P ₄ =

Circuit n° 2		Nom		
V=	V ₁ =	V ₂ =	V ₃ =	V ₄ =
I=	I ₁ =	I ₂ =	I ₃ =	I ₄ =
R _{eq} =	R ₁ =	R ₂ =	R ₃ =	R ₄ =
P _{eq} =	P ₁ =	P ₂ =	P ₃ =	P ₄ =

Circuit n° 3		Nom		
V=	V ₁ =	V ₂ =	V ₃ =	V ₄ =
I=	I ₁ =	I ₂ =	I ₃ =	I ₄ =
R _{eq} =	R ₁ =	R ₂ =	R ₃ =	R ₄ =
P _{eq} =	P ₁ =	P ₂ =	P ₃ =	P ₄ =

Circuit n° 4		Nom		
V=	V ₁ =	V ₂ =	V ₃ =	V ₄ =
I=	I ₁ =	I ₂ =	I ₃ =	I ₄ =
R _{eq} =	R ₁ =	R ₂ =	R ₃ =	R ₄ =
P _{eq} =	P ₁ =	P ₂ =	P ₃ =	P ₄ =

Circuit n° 5		Nom		
V=	V ₁ =	V ₂ =	V ₃ =	V ₄ =
I=	I ₁ =	I ₂ =	I ₃ =	I ₄ =
R _{eq} =	R ₁ =	R ₂ =	R ₃ =	R ₄ =
P _{eq} =	P ₁ =	P ₂ =	P ₃ =	P ₄ =